

### AD7266 SAR ADC in DC-Coupled Differential and Single-Ended Applications


#### CIRCUIT FUNCTION AND BENEFITS

The driver circuits shown in this circuit note are optimized for dc-coupled applications requiring low distortion and low noise performance. This drive circuit ensures that the maximum AD7266 performance is achieved by providing adequate settling time, low distortion, and low output impedance.
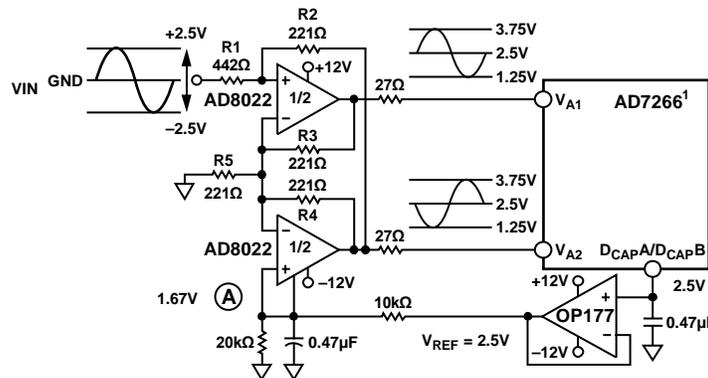
#### CIRCUIT DESCRIPTION

In applications where the signal source has high impedance, it is recommended to buffer the analog input signal before applying it to the switched capacitor inputs of the AD7266. This buffer isolates the source from the transient currents that appear at the

input of the analog-to-digital converter (ADC). A dual op amp pair can be used to directly couple a differential signal to one of the analog input pairs of the AD7266. The AD8022 is an ideal choice for the dual op amp and has low power (4.0 mA per amplifier), low noise (2.5 nV/√Hz at 100 kHz), and low distortion (110 dB spurious-free dynamic range (SFDR) at 200 kHz). The AD7266 has a specified minimum acquisition time of 90 ns with a supply voltage of 5 V. This acquisition time is the time from when the device enters track mode until the next conversion is initiated. The op amp selected must have adequate settling time to meet the acquisition time requirements of the AD7266 and achieve the specified performance.



<sup>1</sup>ADDITIONAL PINS OMITTED FOR CLARITY.

Figure 1. AD8022 DC-Coupled Circuit to Convert a Bipolar Single-Ended Signal into a Unipolar Differential Signal (Simplified Schematic; Decoupling and All Connections Not Shown)

**TABLE OF CONTENTS**

|                                    |   |                        |   |
|------------------------------------|---|------------------------|---|
| Circuit Function and Benefits..... | 1 | Common Variations..... | 3 |
| Circuit Description.....           | 1 | References.....        | 4 |
| Revision History .....             | 2 |                        |   |

**REVISION HISTORY**

**11/2017—Rev. A to Rev. B**

|   |           |
|---|-----------|
| Document Title Changed from CN0039 to AN-1499 ..... | Universal |
| Changes to Circuit Description Section .....        | 1         |
| Changes to References Section .....                 | 4         |

**11/2009—Rev. 0 to Rev. A**

|                                     |           |
|-------------------------------------|-----------|
| Updated Format.....                 | Universal |
| Changes to Circuit Note Title ..... | 1         |

**11/2008—Revision 0: Initial Release**

The circuit configuration shown in Figure 1 shows how an [AD8022](#) op amp can convert a bipolar single-ended signal into a unipolar differential signal that can be applied directly to the [AD7266](#) analog inputs. The circuit not only performs the single-ended to differential conversion but also level shifts the output signal to match the ADC input range. The voltage applied to Point A in Figure 1 sets up the common-mode voltage for each half of the [AD8022](#). The 10 k $\Omega$ /20 k $\Omega$  divider generates this voltage (1.67 V) from the [AD7266](#) 2.5 V internal reference. If using the on-chip 2.5 V reference on the [AD7266](#) elsewhere in a system (as shown in Figure 1 and Figure 2), the output from  $D_{CAPA}$  and  $D_{CAPB}$  must first be buffered. Use the [OP177](#), which features a high precision performance, as a reference buffer.

The primary negative feedback path is provided by Resistor R2 to Resistor R1, and the gain from  $V_{IN}$  to  $V_{A2}$  is set by the ratio of Resistor R2 to Resistor R1. In this case, the ratio is 0.5. The common-mode voltage of 1.67 V at the input of the upper half of the [AD8022](#) produces an output common-mode voltage at  $V_{A2}$  of  $(1 + R2/R1) \times 1.67 \text{ V} = 2.5 \text{ V}$ . Localized feedback supplied by Resistor R3 and Resistor R4 produce a signal at  $V_{A1}$ , which is 180° out of phase with the signal at  $V_{A2}$ .

When the input voltage is zero,  $V_{A1}$  and  $V_{A2}$  must be 2.5 V. This voltage requires a current in both R3 and R4 of

$$(2.5 \text{ V} - 1.67 \text{ V})/221 \Omega = 3.76 \text{ mA}$$

The current through R5 is, therefore,  $2 \times 3.76 \text{ mA} = 7.52 \text{ mA}$ . Therefore, R5 must be equal to R3 and R4 to force the common-mode voltage at  $V_{A1}$  to be 2.5 V.

The [AD7266](#) can have a total of 12 single-ended analog input channels. The analog input range can be programmed to be either 0 V to  $V_{REF}$  or 0 V to  $2 \times V_{REF}$ . Figure 2 shows a typical connection diagram when operating the ADC in single-ended mode, where an [AD8022](#) drives a pair of discrete channels. The [AD8021](#) is a high performance single op amp that can be used as an alternative to a dual device in very high performance systems. The absolute value of R is flexible, but it must be chosen to achieve the desired bandwidth of the op amp.

In Figure 1 and Figure 2, the [AD8022](#) operates on dual 12 V supplies, whereas the [AD7266](#) is specified for power supply voltages of 2.7 V to 5.25 V. Ensure the maximum input voltage limits of the [AD7266](#) are not exceeded during transient or power-on conditions (see [MT-036 Tutorial](#)). In addition, the circuit must be constructed on a multilayer PC board with a large area ground plane. Proper layout, grounding, and decoupling techniques must be used to achieve optimum performance (see [MT-031 Tutorial](#), [MT-101 Tutorial](#), and the [EVAL-AD7266](#) evaluation board layout).

## COMMON VARIATIONS

The [OP07D](#), an ultralow offset voltage op amp, is a lower cost alternative to the [OP177](#). It offers similar performance with the exception of the input offset voltage specification.

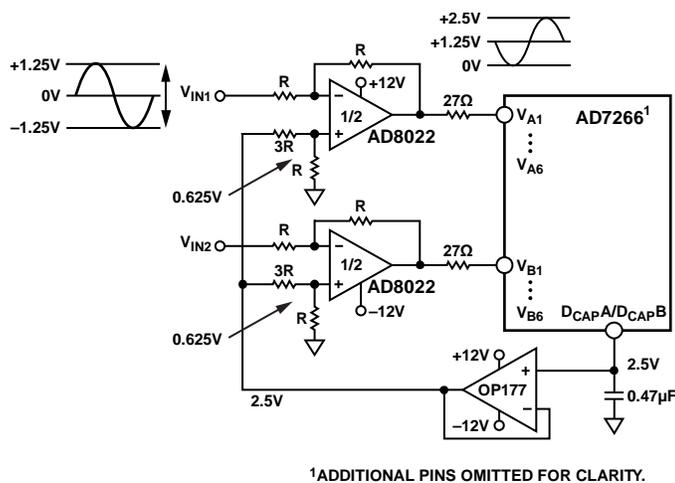


Figure 2. [AD8022](#) DC-Coupled Circuit for a Single-Ended Input Mode of Operation (Simplified Schematic; Decoupling and All Connections Not Shown)

**REFERENCES**

MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of "AGND" and "DGND,"* Analog Devices, Inc.

MT-036 Tutorial, *Op Amp Output Phase-Reversal and Input Over-Voltage Protection,* Analog Devices.

MT-074 Tutorial, *Differential Drivers for Precision ADCs,* Analog Devices.

MT-075 Tutorial, *Differential Drivers for High Speed ADCs Overview,* Analog Devices.

MT-076 Tutorial, *Differential Driver Analysis,* Analog Devices.

MT-101 Tutorial, *Decoupling Techniques,* Analog Devices.